
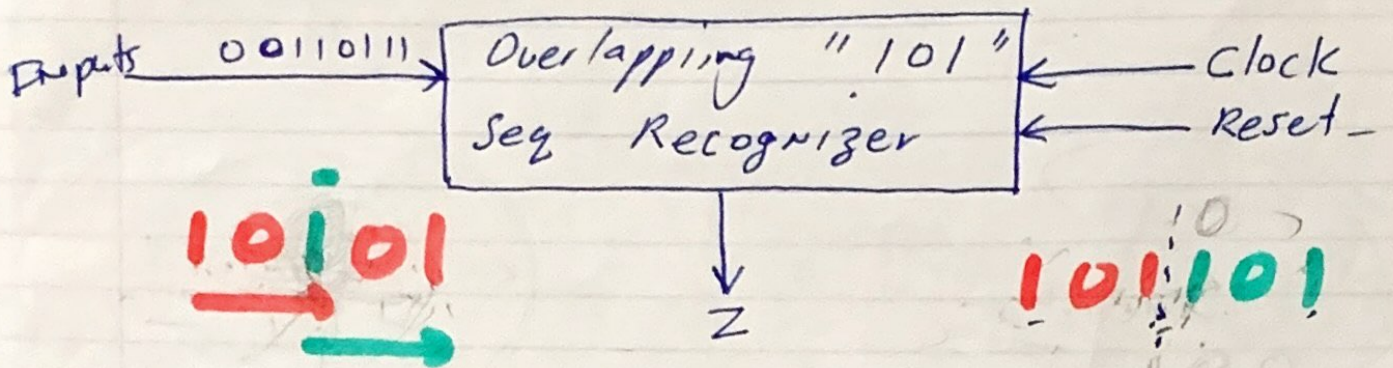


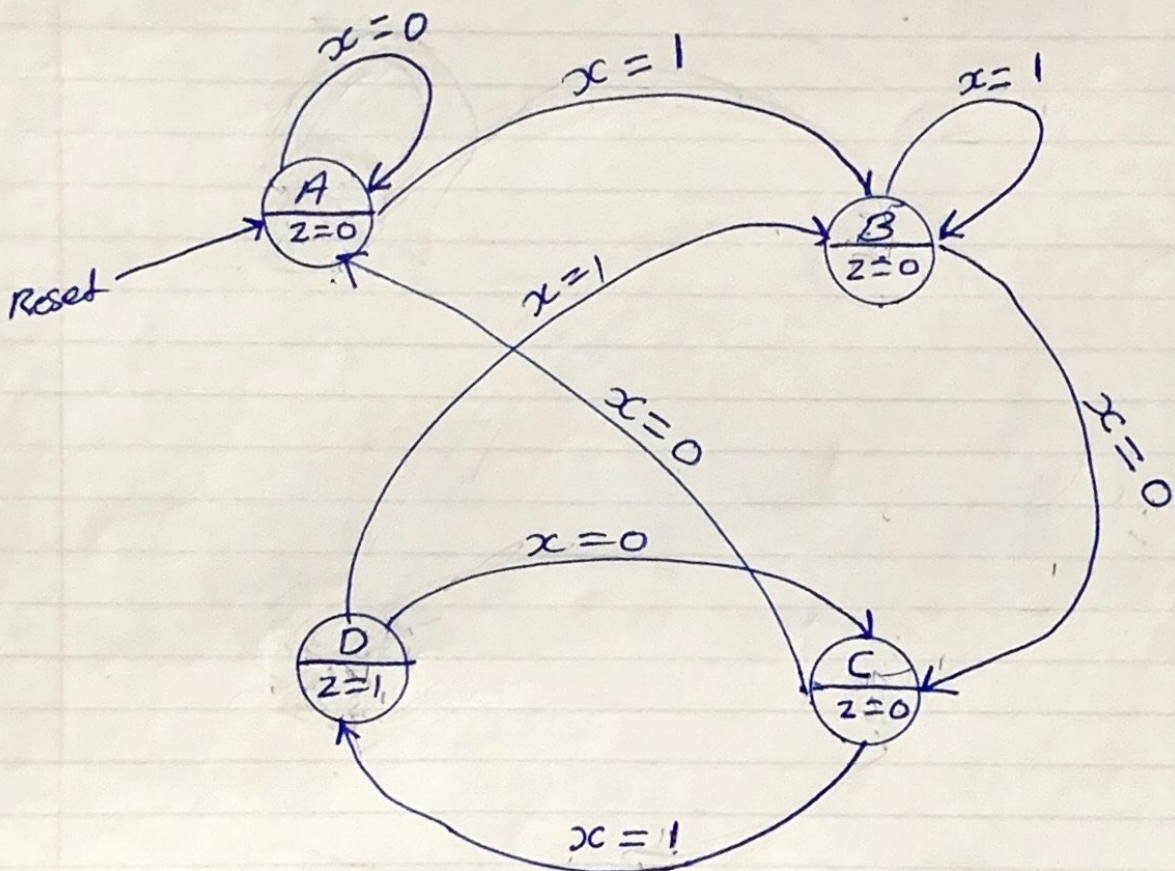Example: Design of a Moore FSM that detects overlapping seq "101"



Step 1: Create a Moore FSD - Finite State Diagram



Design of Moore FSM that detects Overlapping Sequence "101" - Cont.

Step 2: Determine the minimum number of bits required to store the states

$$\text{Number of bits} = \log_2 [K] = \log_2 [4] = 2$$

$K = \#$  of states

Step 3: From the FSD, create the Truth table for NSG & DG

A = 00, B = 01  
C = 10, D = 11

		NSG					
		Current state		Input X	Next state		
		$q_1$	$q_0$	X	$d_1$	$d_0$	
1	A	0	0	0	0	0	A
2		0	0	1	0	1	B
3	B	0	1	0	1	0	C
4		0	1	1	0	1	B
5	C	1	0	0	0	0	A
6		1	0	1	1	1	D
7	D	1	1	0	1	0	C
8		1	1	1	0	1	B


### Step 3 - Cont

Design of a Moore FSM that detects overlapping sequence "101"

Step 3: Create Output Generator (OG)

OG

	Current state			output
	$q_1$	$q_0$		Z
1	0	0	A	0
2	0	1	B	0
3	1	0	C	0
4	1	1	D	1

 

$clk = \text{clock signal}$

Design of a Moore FSM that detects overlapping sequence "101"

Step 4: From the truth table, Determine Min SOP for each of the states - var  $q_1, q_0$ , output  $Z$

$$d_0 = \bar{x} \bar{q}_1 q_0 + x q_1 \bar{q}_0 + \bar{x} q_1 q_0$$

$$= \bar{x} \bar{q}_1 q_0 + \bar{x} q_1 \bar{q}_0 + x q_1 q_0$$

$$= \bar{x} (\bar{q}_1 q_0 + q_1 \bar{q}_0) + x q_1 q_0$$

$$q_0 = 0 \quad q_0 = 1$$

$$\downarrow$$

$$q_0$$

Complement Law  
 $q_0 (\bar{q}_1 + q_1)$   
 $q_0 \cdot 1$   
 $q_0$

$$= \bar{x} q_0 + x q_1 \bar{q}_0$$

$$d_1 = \bar{x} q_0 + x q_0 \bar{q}_0$$

$$d_0 = x; \quad Z = q_1 q_0 \checkmark$$


$$\bar{q}_1 q_0 + q_1 q_0 \Leftrightarrow q_0$$

$q_0 = 0 \Rightarrow$  whole expression = 0


$$\bar{q}_1 \cdot 0 + q_1 \cdot 0 =$$

Design of a Moore FSM that Detects "101" Sequence

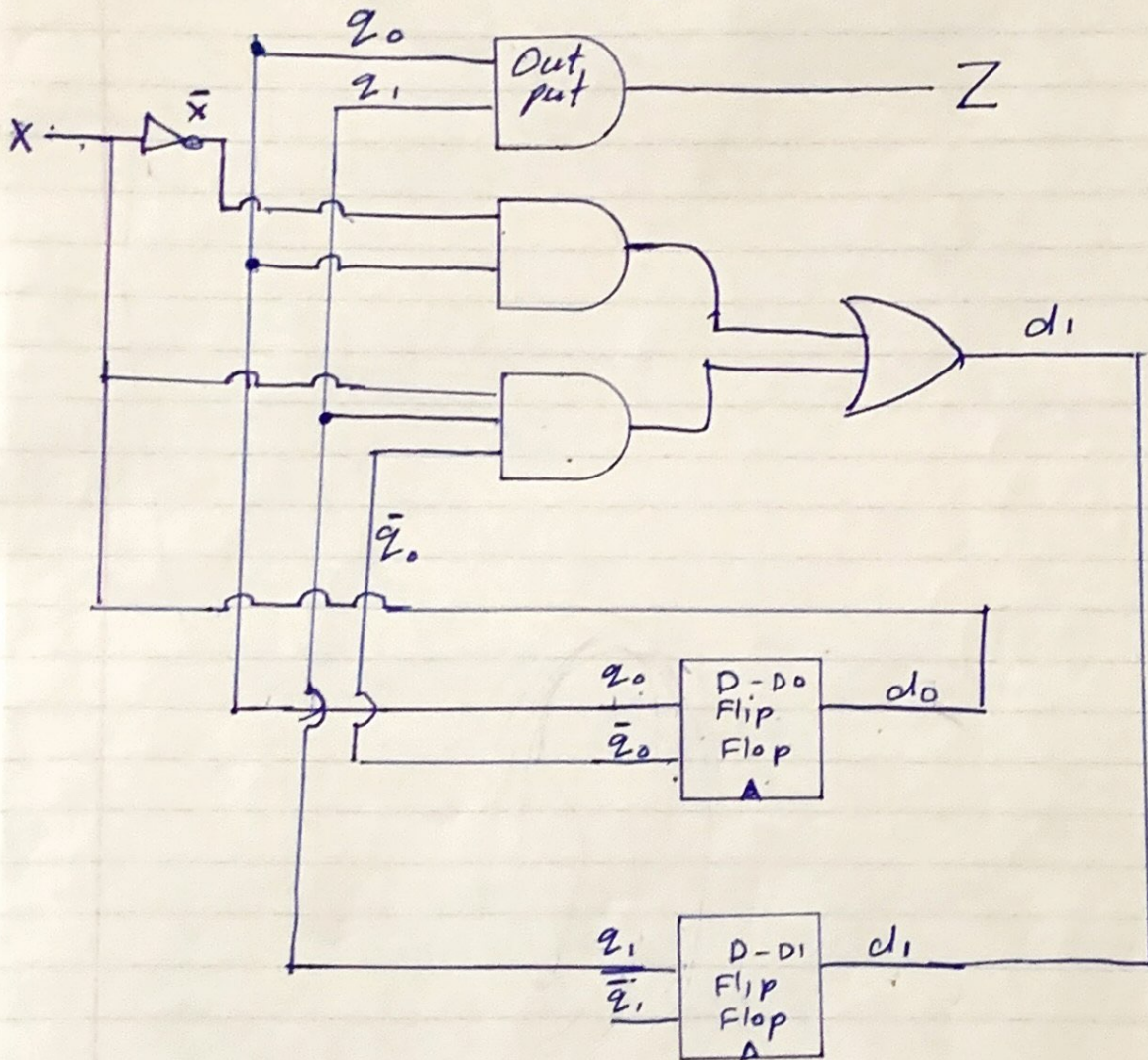Step 5: Build or design the circuit that detects sequence "101"



# D Flip Flops

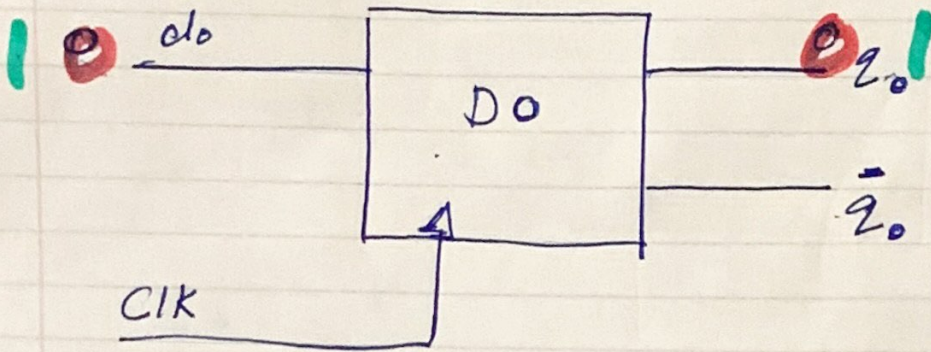

CLK = Clock

$d_0$  = Input (1 bit)


$q_0$  = Output

$\bar{q}_0$  = Inverted Output

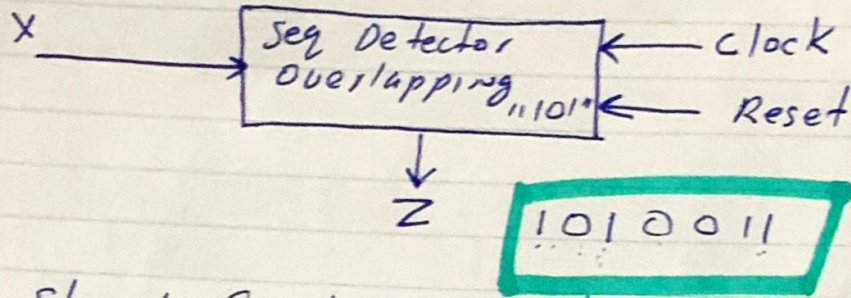
# Design of Mealy FSM - Overlapping

Sequence "101"

\* Mealy output is assigned to the arcs and not to the states



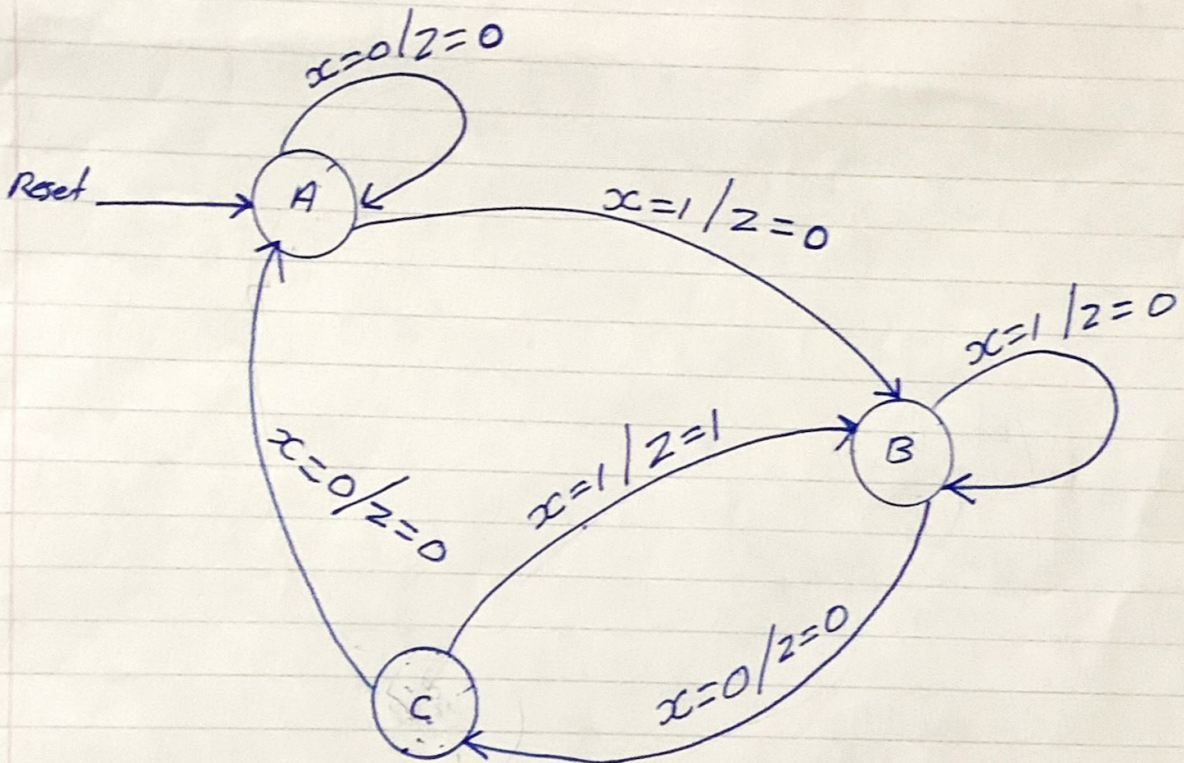Step 1: Create a Mealy Finite State Diagram



# Design of Mealy FSM - Overlapping Sequence "101"

Step 2: Determine the Min number of states/bits required to store the states

$$\text{Number of bits} = \log_2[K] = \log_2[3] \approx 2$$

K = Total # of states

Step 3: From FSD, Create the truth table.  
Let 00 = A, 01 = B, 10 = C, 11 = D.

NSG/OG

	Current States	Input		Next state		Z	
		$q_1$	$q_0$	$x$	$d_1$ $d_0$		
1	A	0	0	0	0 0	A	0
2		0	0	1	0 1	B	0
3	B	0	1	0	1 0	C	0
4		0	1	1	0 1	B	0
5	C	1	0	0	0 0	A	0
6		1	0	1	0 1	B	1
7	D	1	1	0	d d	d	d
8		1	1	1	d d	d	d




# Design of Mealy FSM - Overlapping Sequence "101"

Step 4: Determine the logical Expression


$$d_1 = q_0 \bar{x} \quad ; \quad d_1 = q_0 \bar{q}_1 \bar{x}$$

$$d_0 = x \quad z = q_1 x$$

Step 5: Draw the Circuit Diagram

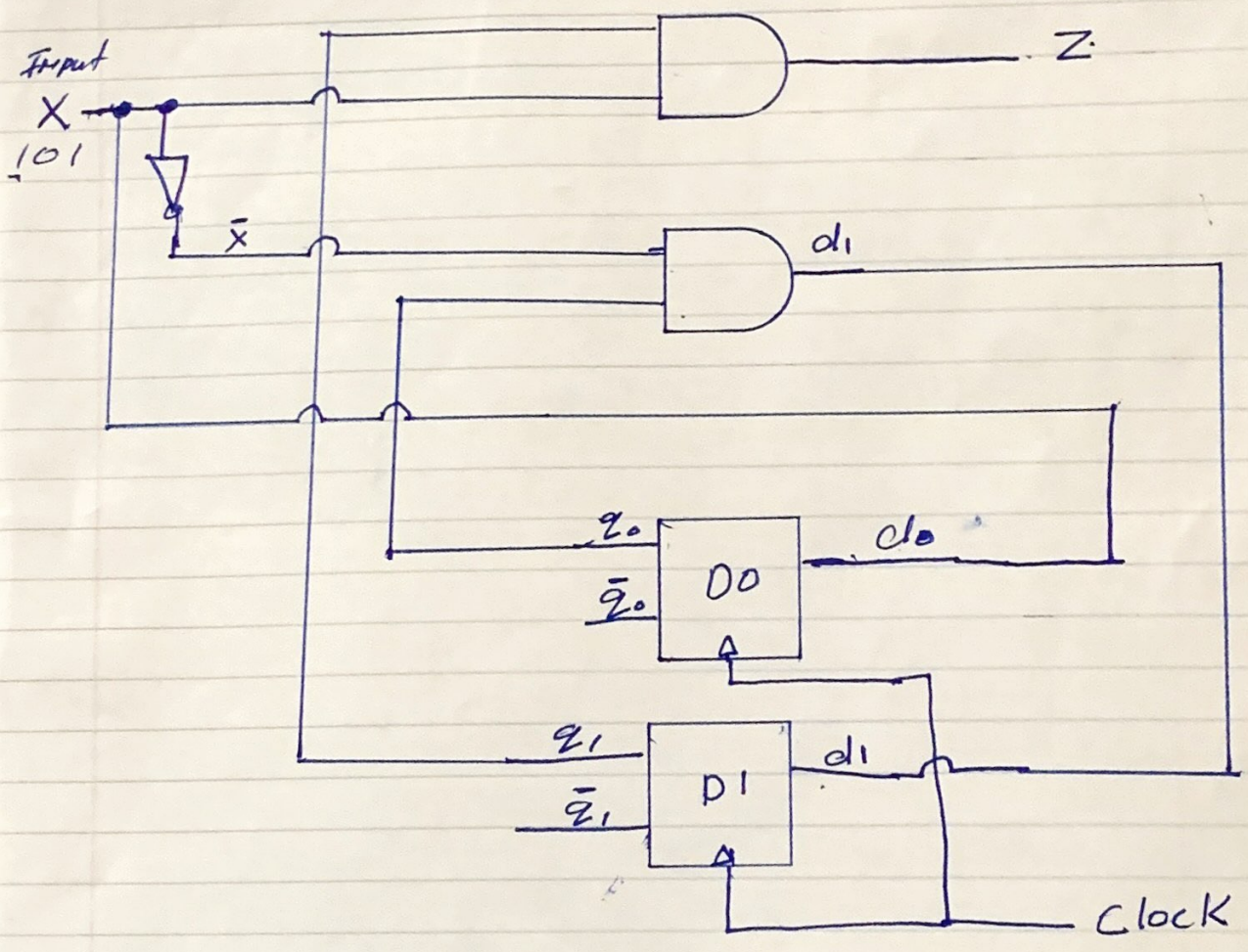

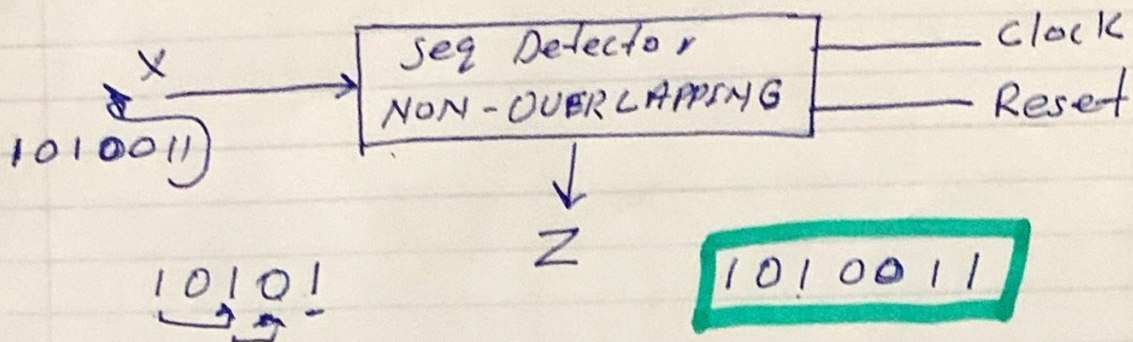Example: Design of Mealy Finite State machine that detects NON-OVERLAPPING Sequence "101"



Step 1: Create a mealy FSD - Finite state Diagram.

Let  $A = 00$ ,  $B = 01$ ,  $C = 10$ ,  $D = 11$

